

# Network Analysis

Network:

Combination (Series + Parallel) of passive and active elements, such as, R, L & C (passive elements) and Voltage Current Source, fixed or controlled (active elements), is called a Network.

Networks are equivalent models of (2) an actual equipment or a system (such as power system).

Analysis means to analyze or evaluate different parameters, e.g.  $i$ ,  $v$ ,  $P$ ,  $Q$ ,  $S$ , P.f under normal or abnormal condition, or we say, steady-state or transient conditions.

---


Define  $R$ ,  $L$ ,  $C$  and equations Associates.

$R \rightarrow$  Resistor,  $\rightarrow$  Resistance,  $\rightarrow$  ohm  $\rightarrow \Omega$   
Conductors  $\rightarrow$  Define, Low Resistance  
Insulator  $\rightarrow$  Define, High Resistance  
Both are important for each other.

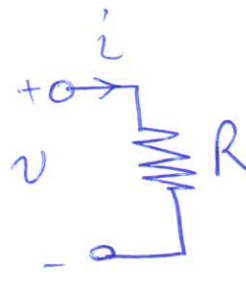Example of Conductors  $\rightarrow$  Copper  
 $\rightarrow$  Aluminium  
 $\rightarrow$  Zn  
 $\rightarrow$  Gold  
 $\rightarrow$  Silver  
 $\rightarrow$  Alloys,  
 $\rightarrow$  many other

opposition to flow of electrical current is called Resistance.

Element which opposes flow of Electric current is called Resistor



$$V = iR$$

$$R = \frac{V}{i} \text{ (ohm's law)}$$


(3)

$$P = I^2 R$$

R → Constant by keeping temperature constant.

$$R_t = R_0 (1 + \alpha t) \quad \text{Conductor}$$
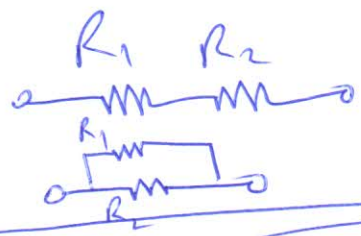
$$R_t = R_0 (1 - \alpha t) \quad \text{Insulator}$$



$$R_{eq} = R_1 + R_2$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

ideal  $P = 0$

$$E = \frac{1}{2} Li^2$$

$$\psi = Li$$

$$i = \frac{\psi}{L}$$

$$E = \frac{1}{2} \frac{\psi^2}{L}$$



Energy is stored in Magnetic field  
 $Li = N\Phi$

$$L = \frac{N\Phi}{i}$$

$$V = L \frac{di}{dt}$$

$$i = \frac{1}{L} \int^t V \cdot dt$$

$$i = I_0 + \frac{1}{L} \int^t V \cdot dt$$

$$V = \frac{d\psi}{dt}$$

$$\psi = Li$$

$$V = \frac{d}{dt} (Li)$$

$$V = L \frac{di}{dt} + i \frac{dL}{dt}$$

Faraday's Law

e.m.f induced is equal to rate of change of flux linkages.

Element which opposes any change in current abruptly or instantaneously is called L

$L_{eq} = L_1 + L_2$


$$V = L \frac{di}{dt}$$

for L = constant



$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$

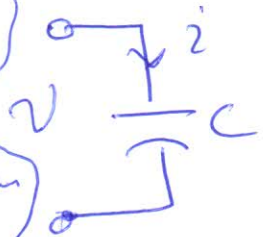Element which opposes abrupt/instantaneous change in voltage called capacitor



$$i = C \frac{dv}{dt}$$
$$V = \frac{1}{C} \int_{-\infty}^t i \cdot dt$$


$$V = V_0 + \frac{1}{C} \int_0^t i \cdot dt$$

$i = \frac{dq}{dt}$  = rate of change of charge is current.


$$i = C \frac{dv}{dt} + v \cdot \frac{dc}{dt}$$

$$i = C \frac{dv}{dt}$$


C = Constant

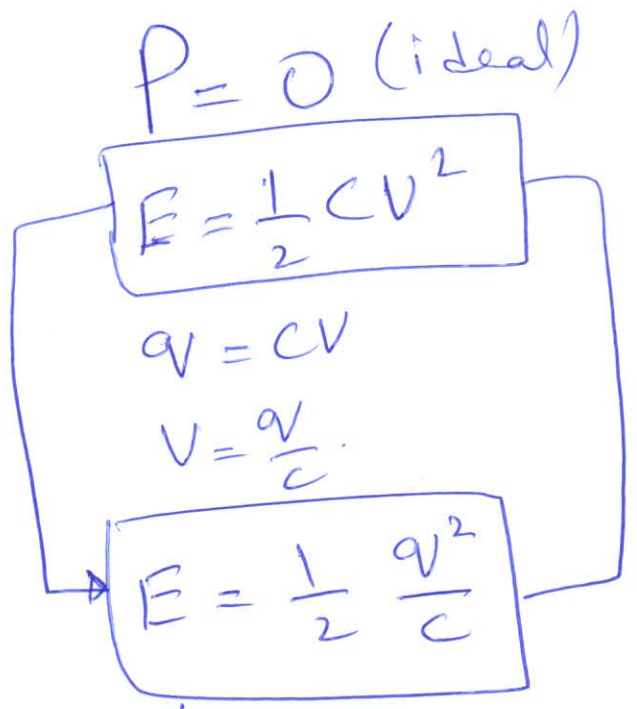

Energy is stored in Electric field

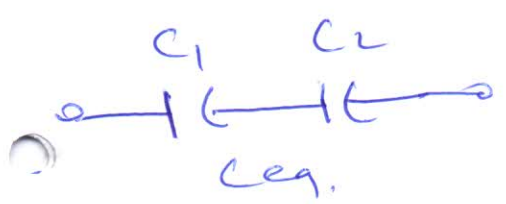



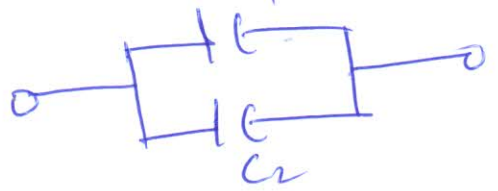
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$



$$C_{eq} = C_1 + C_2$$

99% Load is Inductive.

(a) Single-phase load.

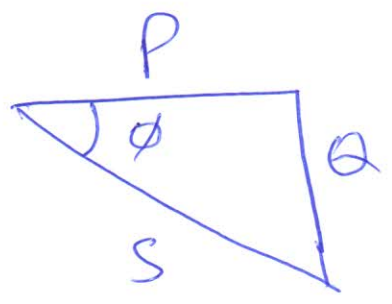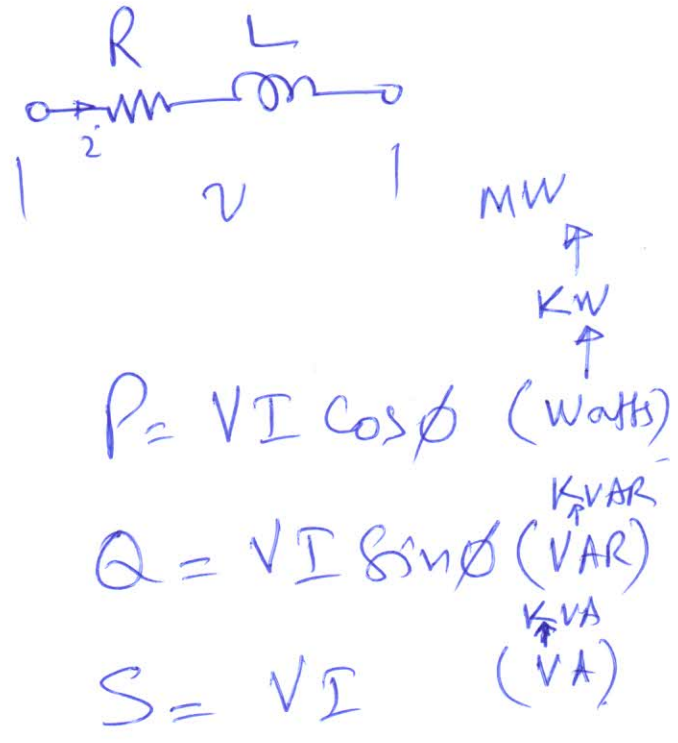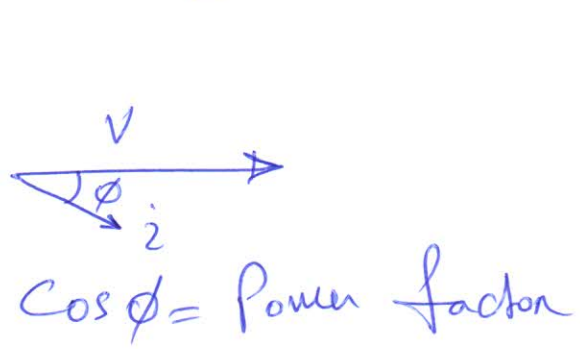



Fan, Tube light, A-C, Induction Motors, etc., etc.

(b) Three-phase load

Balance  $\Rightarrow I_1 = I_2 = I_3$   
 Un Balance  $\Rightarrow I_1 \neq I_2 \neq I_3$




Connections

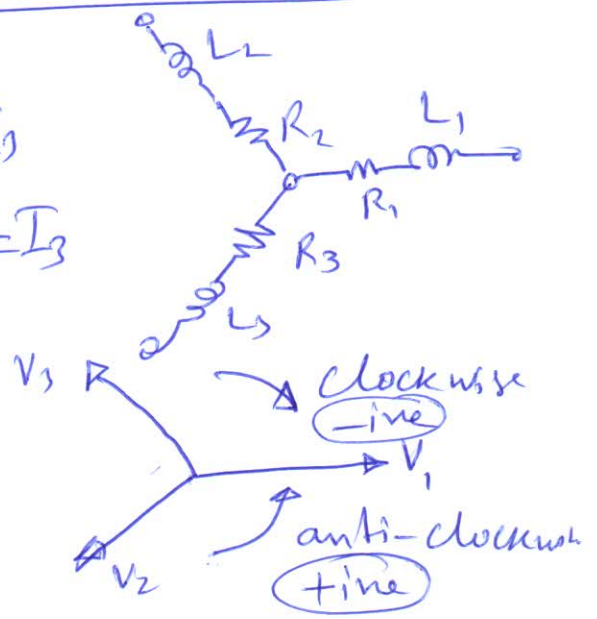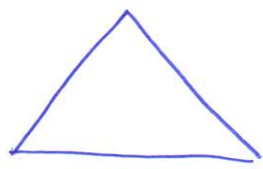



$$I_{ph} = I_L$$

Y-Connections

$$V_{ph} = \frac{V_L}{\sqrt{3}}$$

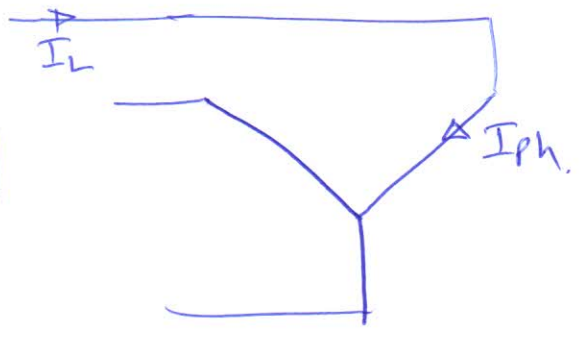
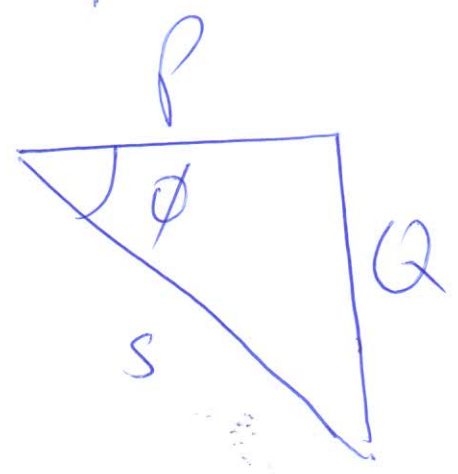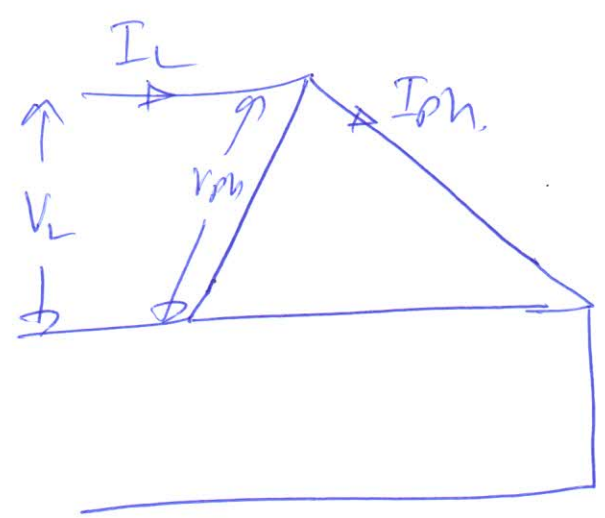
$$V_{ph} = V_L$$
$$I_{ph} = \frac{I_L}{\sqrt{3}}$$



$$P = \sqrt{3} V I \cos \phi$$

$$Q = \sqrt{3} V I \sin \phi$$


$$S = \sqrt{3} V I$$

$$P_T = P_A + P_B + P_C$$


# First Order + 2nd order Differential Equations

(7)

First order Differential Equations

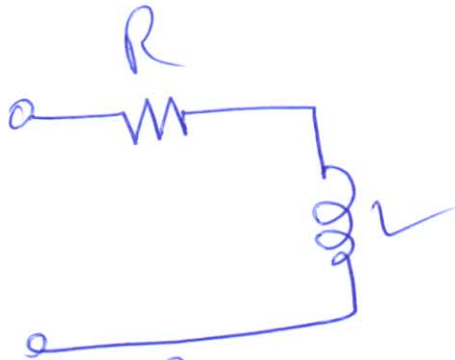


$$v = iR + L \frac{di}{dt}$$

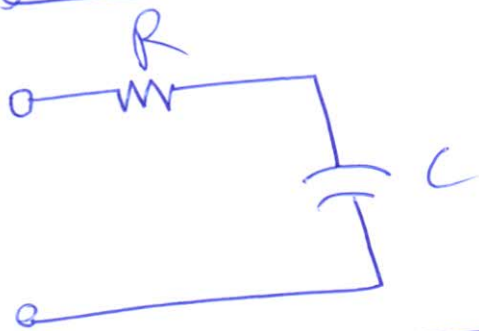

$$v = iR + \frac{1}{C} \int_{-\infty}^t i \cdot dt$$

One Storage element  
First order Differential Equation

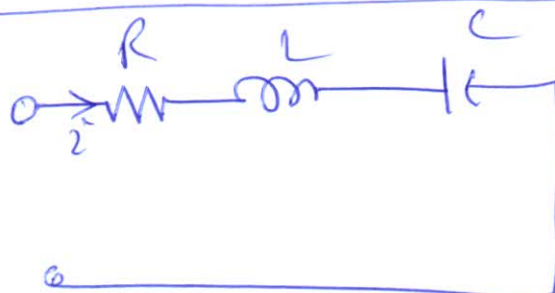Two Storage element  
at least 2nd order Differential Equation



$$v = iR + L \frac{di}{dt} + \frac{1}{C} \int_{-\infty}^t i \cdot dt$$

$$\frac{dv}{dt} = R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{i}{C}$$