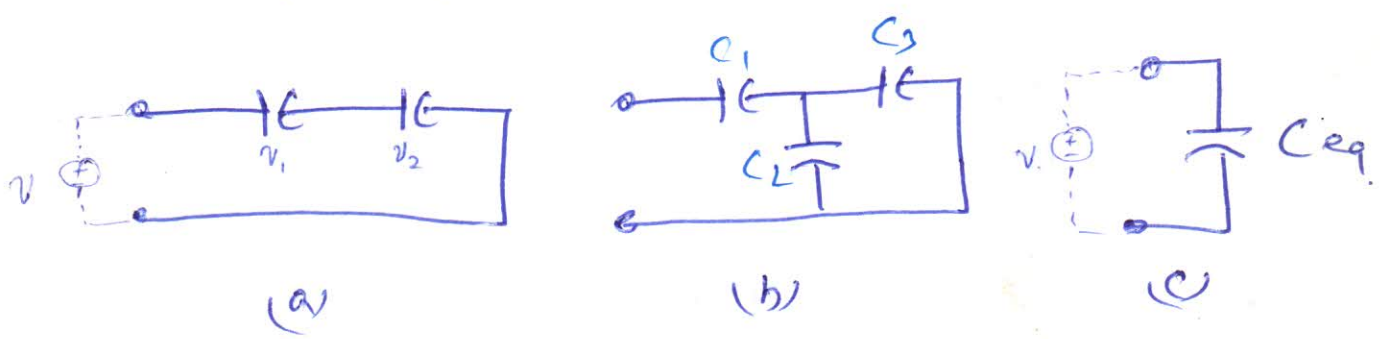


Problems.

3.1 what must be the relationship between C_{eq} and C_1 and C_2 in (a) of the figure of the network if (a) and (c) are equivalent?

Repeat for the network shown in (b).



□ fig. (a) equivalent to fig. (c)

According to K.V. Law.

$$\sum V. Rise = \sum \text{Voltage-drops}$$

from fig. (a) $V = v_1 + v_2$

$$\frac{q}{C_{eq}} = \frac{q}{C_1} + \frac{q}{C_2}$$



$$\left[v_1 = \frac{q}{C_1}, v_2 = \frac{q}{C_2} \right]$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\text{or } \frac{1}{C_{eq}} = \frac{C_1 + C_2}{C_1 C_2}$$

$$\boxed{C_{eq} = \frac{C_1 C_2}{C_1 + C_2}}$$

b

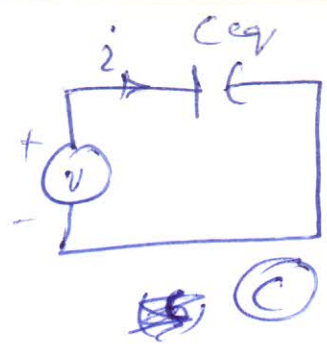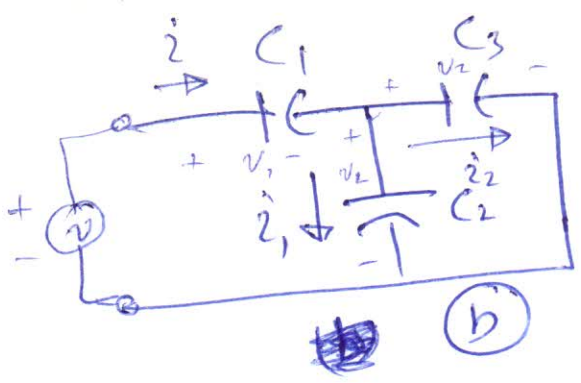

$$i = i_1 + i_2$$

$$i_1 = C_1 \frac{dv_1}{dt}, \quad i_2 = C_2 \frac{dv_2}{dt}, \quad i_2 = C_3 \frac{dv_3}{dt}$$

where $v_1 =$ voltage across C_1 , $v_2 =$ across C_2 and $v_3 =$ voltage across C_3 .

$$C_1 \cdot \frac{dv_1}{dt} = C_2 \frac{dv_2}{dt} + C_3 \frac{dv_3}{dt}$$

$$v_2 = v_3 = v_2 \text{ (say)}$$

$$\text{i.e. } \frac{dv_2}{dt} = \frac{dv_3}{dt}$$

$$C_1 \cdot \frac{dv_1}{dt} = (C_2 + C_3) \frac{dv_2}{dt}$$

So

$$\boxed{\frac{dv_2}{dt} = \frac{C_1}{C_2 + C_3} \cdot \frac{dv_1}{dt}} \rightarrow \textcircled{1}$$

from fig. (b):

$$v = v_1 + v_2$$

$$\frac{dv}{dt} = \frac{dv_1}{dt} + \frac{dv_2}{dt}$$

But the value of $\frac{dv_2}{dt}$ from previous equation is

$$\frac{dv_2}{dt} = \frac{C_1}{C_2+C_3} \cdot \frac{dv_1}{dt}$$

$$\frac{dv}{dt} = \frac{dv_1}{dt} + \frac{C_1}{C_2+C_3} \cdot \frac{dv_1}{dt}$$

$$= \frac{dv_1}{dt} \left(1 + \frac{C_1}{C_2+C_3} \right) = \frac{dv_1}{dt} \left(\frac{C_2+C_3+C_1}{C_2+C_3} \right)$$

So

$$\boxed{\frac{dv_1}{dt} = \frac{C_2+C_3}{C_1+C_2+C_3} \frac{dv}{dt}} \rightarrow \textcircled{2}$$

from eq. (b) $i = C_1 \frac{dv_1}{dt}$,

from eq. (c) $i = C_{eq} \cdot \frac{dv}{dt}$

$$i = i$$

$$C_1 \frac{dv_1}{dt} = C_{eq} \cdot \frac{dv}{dt}$$




$$\boxed{\frac{dv_1}{dt} = \frac{C_{eq}}{C_1} \cdot \frac{dv}{dt}} \rightarrow \textcircled{3}$$

Put $\textcircled{3}$ into equation $\textcircled{2}$



$$\frac{C_{eq}}{C_1} \cdot \frac{dV}{dt} = \frac{C_2 + C_3}{C_1 + C_2 + C_3} \frac{dV}{dt}$$

$$C_{eq} = \frac{C_1 (C_2 + C_3)}{C_1 + C_2 + C_3}$$

Prob: 3.2 what must be the relationship between L_{eq} and L_1, L_2 and M for networks of (a) and of (b) to be equivalent to that of (c)?

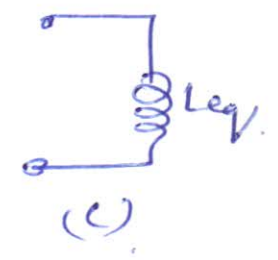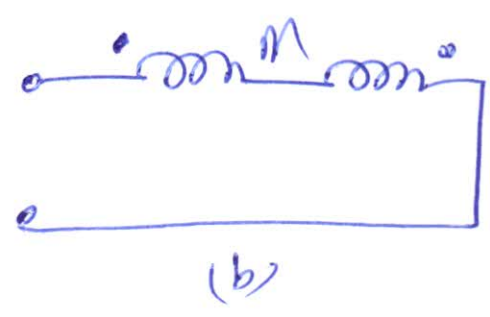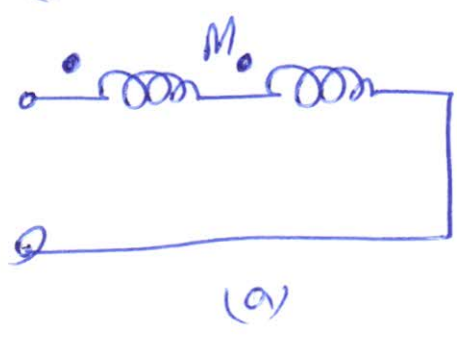

Part I

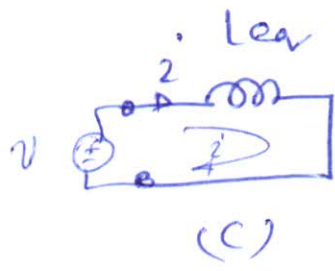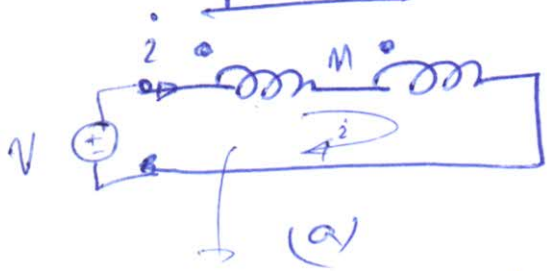

Apply K.V. Law from fig. (a)

$$V = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + M_{12} \frac{di}{dt} + M_{21} \cdot \frac{di}{dt}$$

Now let $M_{12} = M_{21} = M$

$$V = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + 2M \frac{di}{dt} \rightarrow \textcircled{1}$$

from fig. (c)

$$V = L_{eq} \cdot \frac{di}{dt} \rightarrow \textcircled{2}$$



Comparing ① & ②

162

$$L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + 2M \frac{di}{dt} = L_{eq} \frac{di}{dt}$$

$$L_{eq} = L_1 + L_2 + 2M$$

Part - II

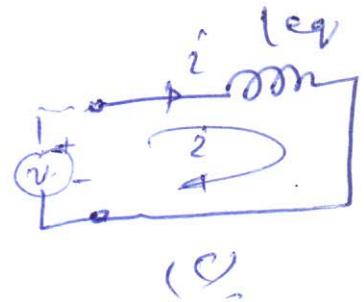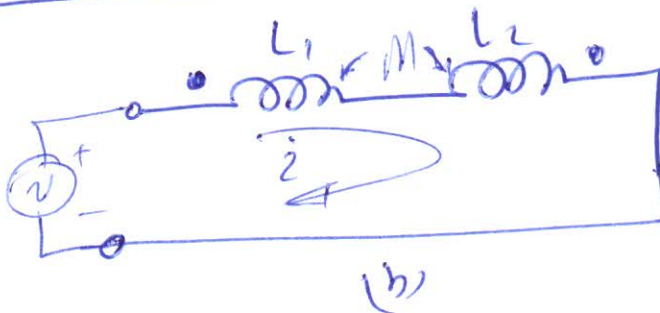

from (b), Apply K.V-Law

$$v = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} - M_{12} \frac{di}{dt} - M_{21} \frac{di}{dt}$$

$$\text{Let } M_{12} = M_{21} = M.$$

$$v = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} - 2M \frac{di}{dt} \rightarrow \text{③}$$


from ①

$$v = L_{eq} \frac{di}{dt} \rightarrow \text{④}$$


Equating ③ & ④

$$L_{eq} = L_1 + L_2 - 2M$$

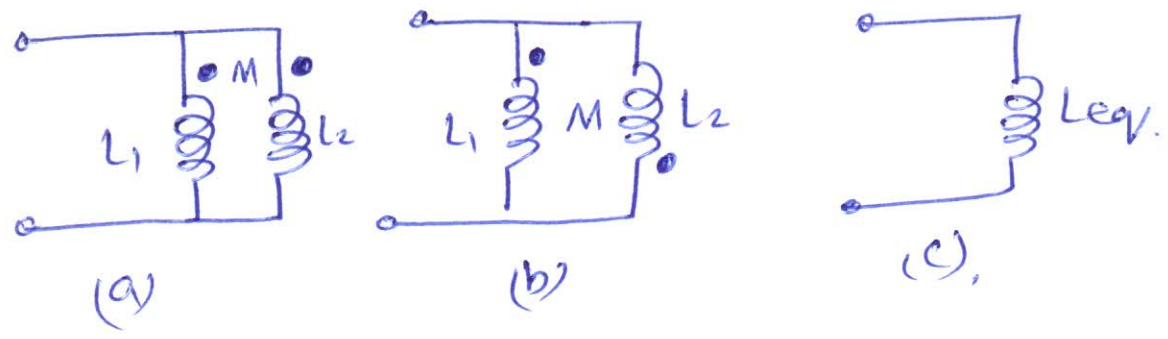Prob: 3.3 Repeat prob: 3.2 for the three networks shown in the accompanying figure. (163)



Part-I

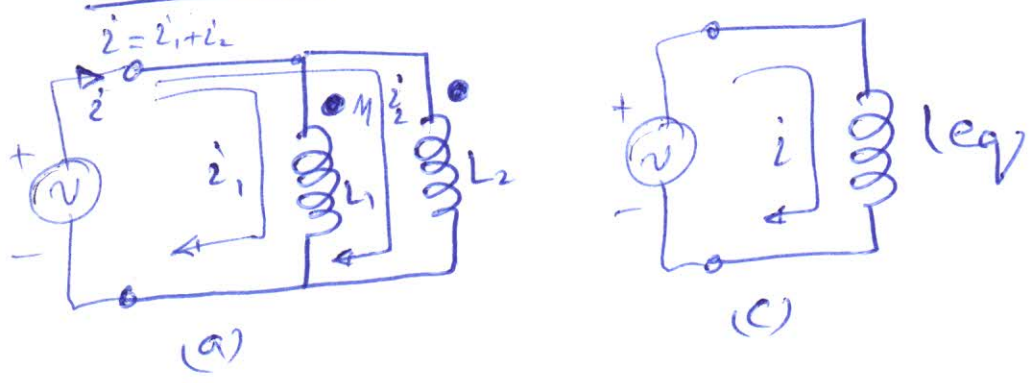

$$v = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad \text{--- (1)}$$

$$v = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \quad \text{--- (2)}$$

Equation (1) and (2)

$$L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$$\frac{di_2}{dt} (L_2 - M) = \frac{di_1}{dt} (L_1 - M)$$

i.e. $\frac{di_2}{dt} = \left(\frac{L_1 - M}{L_2 - M} \right) \frac{di_1}{dt}$

from eq: (1) $V = L_{eq} \cdot \frac{di}{dt}$

$$i = i_1 + i_2$$

$$\frac{di}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt}$$

$$V = L_{eq} \left[\frac{di_1}{dt} + \frac{di_2}{dt} \right] \rightarrow (2)$$

from (2) $V = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$

So, (2) becomes,

$$L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} = L_{eq} \left[\frac{di_1}{dt} + \frac{di_2}{dt} \right]$$

Put $\frac{di_2}{dt} = \left(\frac{L_1 - M}{L_2 - M} \right) \frac{di_1}{dt}$

$$L_2 \left[\frac{L_1 - M}{L_2 - M} \right] \frac{di_1}{dt} + M \frac{di_1}{dt} = L_{eq} \left[\frac{di_1}{dt} + \left(\frac{L_1 - M}{L_2 - M} \right) \frac{di_1}{dt} \right]$$

OR, $L_2 \left(\frac{L_1 - M}{L_2 - M} \right) + M = L_{eq} \left[1 + \frac{L_1 - M}{L_2 - M} \right]$

OR $L_2 \left(\frac{L_1 - M}{L_2 - M} \right) + M = L_{eq} \left[\frac{L_1 + L_2 - 2M}{L_2 - M} \right]$



OR $\frac{L_2 (L_1 - M) + M(L_2 - M)}{L_2 - M} = L_{eq} \left(\frac{L_1 + L_2 - 2M}{L_2 - M} \right)$

OR $L_{eq} = \frac{L_1 L_2 - L_2 M + L_2 M - M^2}{L_1 + L_2 - 2M}$

finally $L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$

~~Handwritten scribbles and crossed-out text at the bottom left.~~

Part - II

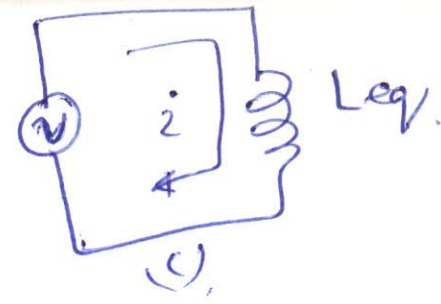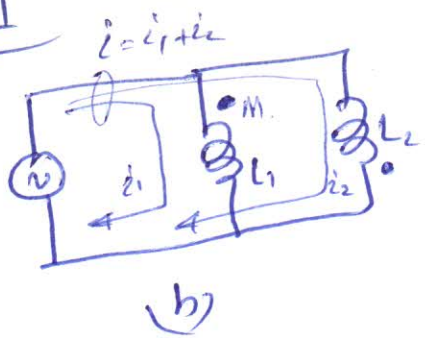

Loop-1, $V = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$ — (1)

Loop-2 $V = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$ — (2)

Equating (1) and (2)

$$L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

OR $\frac{di_2}{dt} (L_2 + M) = \frac{di_1}{dt} (L_1 + M)$

OR $\boxed{\frac{di_2}{dt} = \left(\frac{L_1 + M}{L_2 + M} \right) \frac{di_1}{dt}}$

from fig: (c) $V = L_{eq} \cdot \frac{di}{dt}$

But $i = i_1 + i_2$
 $\frac{di}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt}$

So $V = L_{eq} \left[\frac{di_1}{dt} + \frac{di_2}{dt} \right] \rightarrow$ (3)

Also from (2)
 $V = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$

Equating (3) & (2)

$$L_2 \frac{di_2}{dt} - M \frac{di_1}{dt} = L_{eq} \left[\frac{di_1}{dt} + \frac{di_2}{dt} \right] \rightarrow (4)$$

But we know that

$$\frac{di_2}{dt} = \left(\frac{L_1 + M}{L_2 + M} \right) \frac{di_1}{dt}$$

Put this in (4)

$$L_2 \cdot \left(\frac{L_1 + M}{L_2 + M} \right) \frac{di_1}{dt} - M \frac{di_1}{dt} = L_{eq} \left[\frac{di_1}{dt} + \left(\frac{L_1 + M}{L_2 + M} \right) \frac{di_1}{dt} \right]$$

OR $\left(\frac{di_1}{dt} \right)$ is common on both side hence eliminate

$$L_2 \frac{(L_1 + M)}{L_2 + M} - M = L_{eq} \left[1 + \frac{L_1 + M}{L_2 + M} \right]$$

$$\text{OR} \quad \frac{L_2 (L_1 + M) - M (L_2 + M)}{L_2 + M} = L_{eq} \left[\frac{L_2 + M + L_1 + M}{L_2 + M} \right]$$

$$L_{eq} = \frac{L_1 L_2 + L_2 M - L_2 M - M^2}{L_1 + L_2 + 2M}$$

OR


$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$

Prob: 3.4


The network of inductors shown in fig. is composed of a 1-H inductor on each edge of a cube as shown. Show that, with respect to vertices

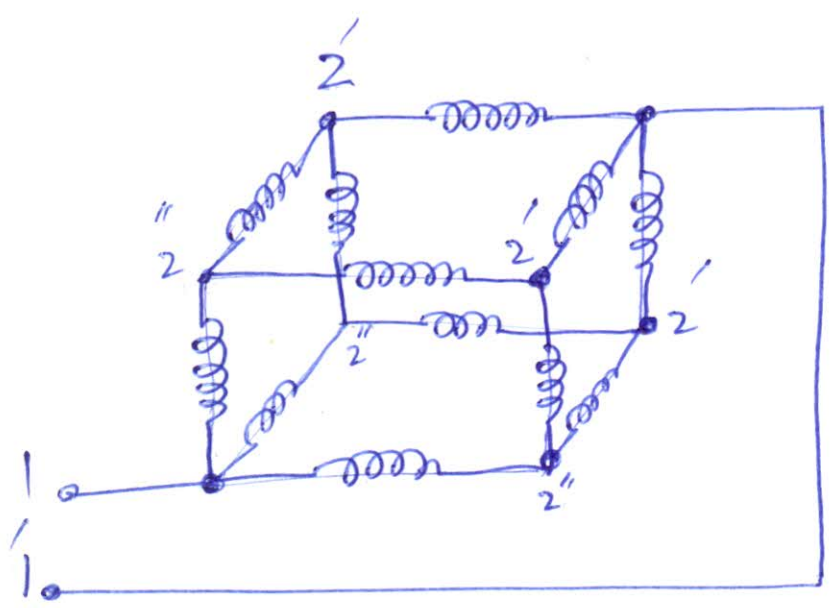(a) and (b), the network is equivalent to that in (b) of the figure when $L_{eq} = \frac{5}{6} H$.

Make use of symmetry in working in this problem, rather than writing Kirchhoff's laws.




(a)

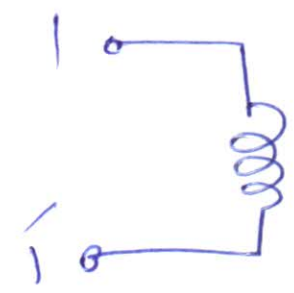

(b)

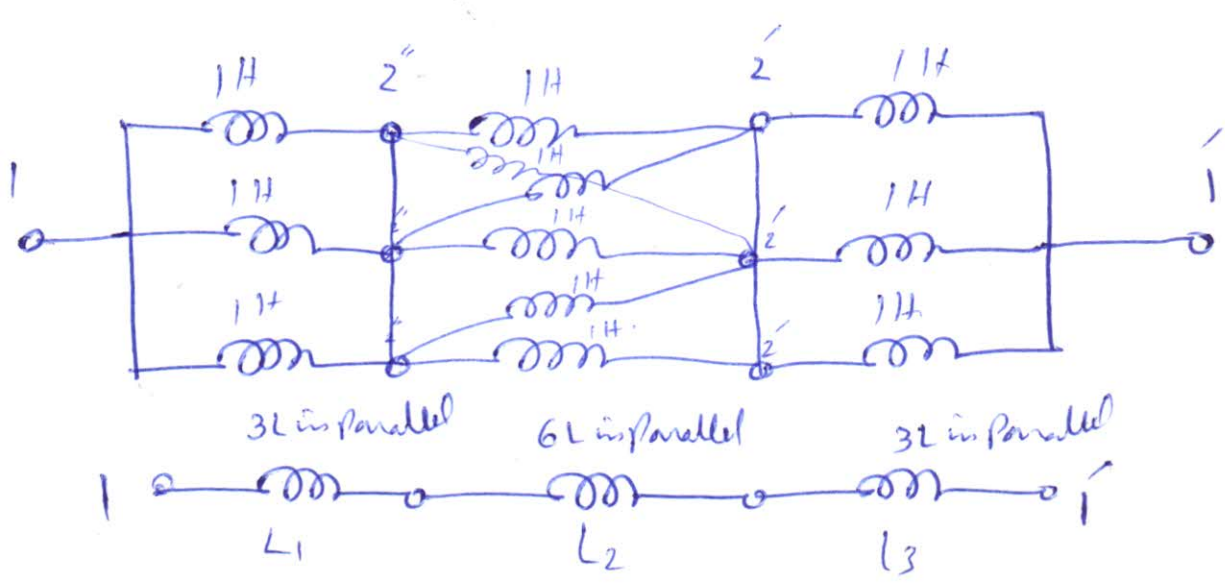Nodes - 2' and Nodes - 2'' are at one potential as each branch is 1-H; therefore they can be short circuited as below.




$$\frac{1}{L_1} = \frac{1}{1} + \frac{1}{1} + \frac{1}{1} = 3$$

$$\frac{1}{L_2} = \frac{1}{1} + \frac{1}{1} + \frac{1}{1} + \frac{1}{1} + \frac{1}{1} + \frac{1}{1} = 6$$

$$\frac{1}{L_3} = \frac{1}{1} + \frac{1}{1} + \frac{1}{1} = 3$$
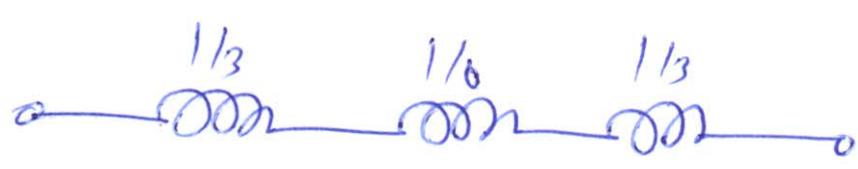
$$L_1 = \frac{1}{3}, L_2 = \frac{1}{6}, L_3 = \frac{1}{3}$$




$$L_{eq} = L_1 + L_2 + L_3 = \frac{1}{3} + \frac{1}{6} + \frac{1}{3} = \frac{2+1+2}{6} = \frac{5}{6} H$$

$$L_{eq} = \frac{5}{6} H$$



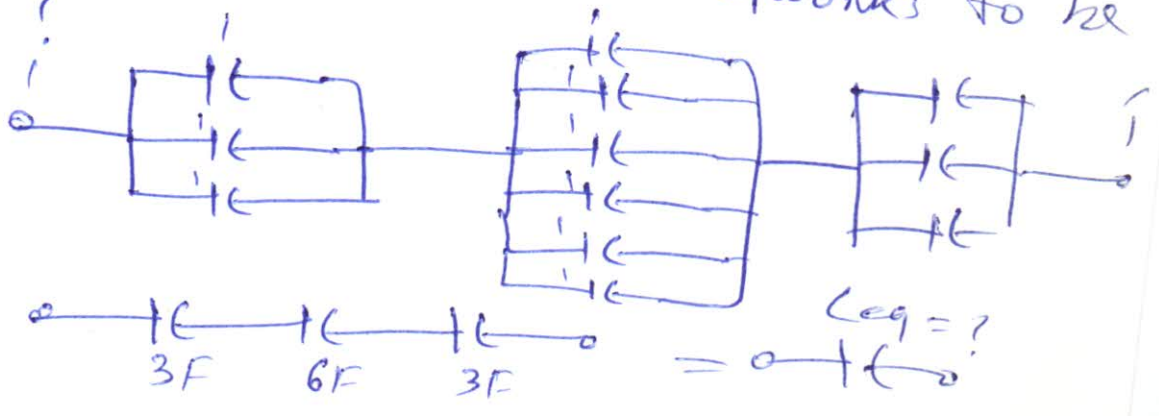Prob: 3.5 In the network of Prob. 3.4, each $\frac{1}{6} H$ inductor is replaced by 1 Farad capacitor and L_{eq} is replaced by C_{eq} . what must be the value of C_{eq} for the two networks to be equivalent?



$$\frac{1}{C_{eq}} = \frac{1}{3} + \frac{1}{6} + \frac{1}{3} = \frac{2+1+2}{6} = \frac{5}{6}$$


$$C_{eq} = \frac{6}{5} F$$

Prob: 3.6

This prob. may be solved using the two Kirchhoff laws and voltage-current relationship for the elements.

At time t_0 after the switch K was closed, it is found that $v_2 = +5V$, You are required to determine the value of $i_2(t_0)$ and $\frac{di_2}{dt}(t_0)$

Sol.

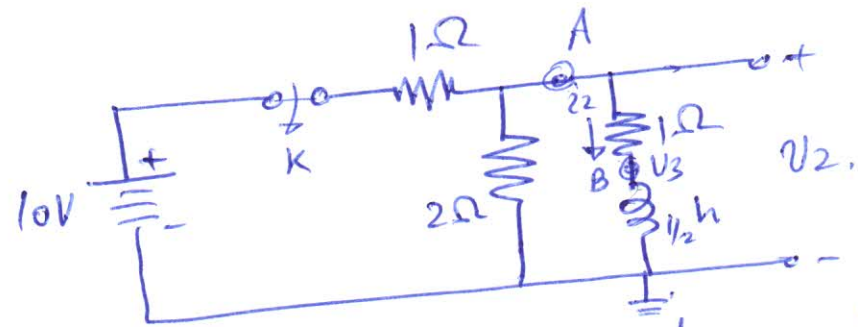

Switch K is closed after time $= t_0$.

$v_2(t_0) = 5V$.

Apply K. Current law and write equation at Node (A)

$$\frac{v_2 - v_3}{1} + \frac{v_2 - 10}{1} + \frac{v_2}{2} = 0 \rightarrow \textcircled{1}$$

Since eq. $\textcircled{1}$ is valid for all times it is also valid for $t = t_0$, $v_2 = 5V$. So equation $\textcircled{1}$ becomes

$$\frac{5 - v_3}{1} + \frac{5 - 10}{1} + \frac{5}{2} = 0$$

$v_3(t_0) = 2.5V$.


$i_2(t_0) = \frac{v_2(t_0) - v_3(t_0)}{1} = \frac{5 - 2.5}{1} = 2.5 \text{ Amperes}$.

Now also V_3 is the voltage across the inductor, i.e. $V_3 = L \frac{di_L}{dt}$ for all times.

$$V_3(t_0) = L \frac{di_L(t_0)}{dt}$$

$$\text{or } \frac{di_L(t_0)}{dt} = \frac{V_3(t_0)}{L} = \frac{2.5}{1/2} = 5 \text{ Amp/sec}$$

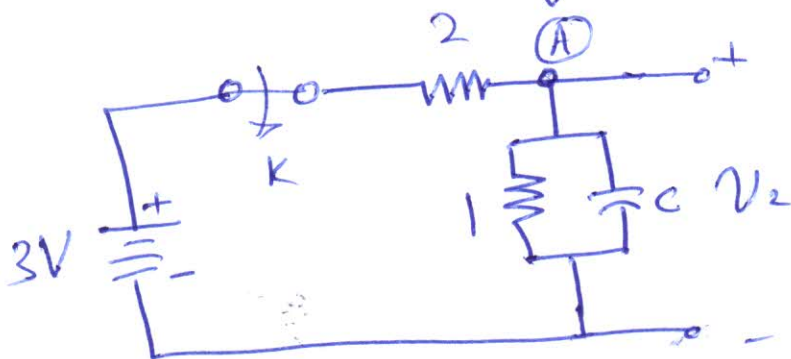Prob: 3.7 This problem is similar to Prob: 3.6. In the network given in the fig, it is given that $V_2(t_0) = 2V$ and $\frac{dV_2}{dt}(t_0) = -10V/\text{sec}$, where t_0 is the time after the switch K was closed. Determine the value of " C ".



Sol:

Writing Nodal equation at (A) by Applying K.C.C.

$$\frac{V_2 - 0}{1} + \frac{V_2 - 3}{2} + C \frac{dV_2}{dt} = 0$$

(Valid for all times)

$$\frac{V_2(t_0)}{1} + \frac{V_2(t_0) - 3}{2} + C \frac{dV_2(t_0)}{dt} = 0$$

Now putting the given values

(171)

$$\frac{2}{1} + \frac{2-3}{2} + C \times (-10) = 0$$

$$2 - \frac{1}{2} - 10C = 0$$

OR

$$10C = \frac{3}{2}$$

OR

$$C = \frac{3}{2 \times 10} = 0.15 \text{ F}$$




$$C = 0.15 \text{ Farads}$$

Prob: 3.8 onwards:

$$A = R = 2$$

$$B = L = 1/2$$

$v_2 = a, b, c, d, e, f.$

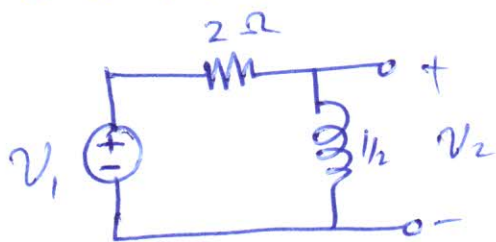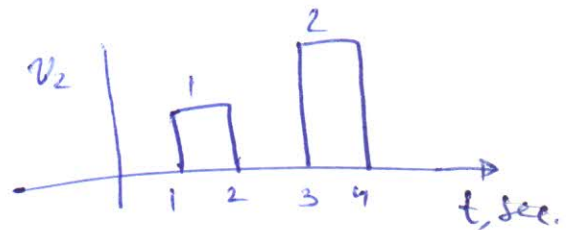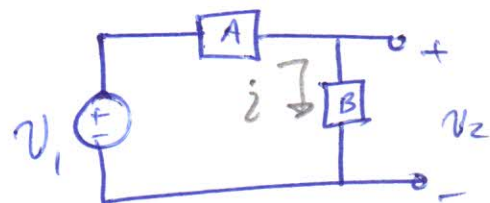

Initial Conditions = 0.

Find s Draw $V_1 = ?$

$$v_1 = i \cdot R + v_2 \checkmark$$

$$\text{But } v_2 = L \frac{di}{dt} \checkmark$$

So

$$v_1 = i \cdot R + L \frac{di}{dt} \checkmark$$

OR

$$v_1 = 2 \cdot i + \frac{1}{2} \frac{di}{dt}$$

↔ (1)